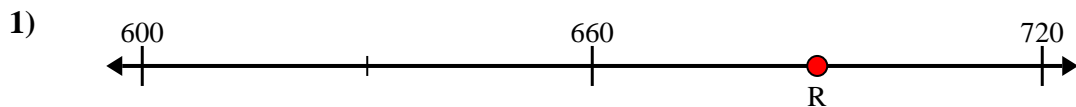





Find the value of R.


Answers



1. _____

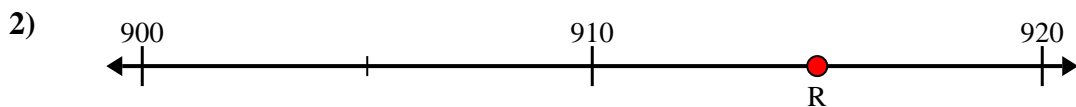


2. _____

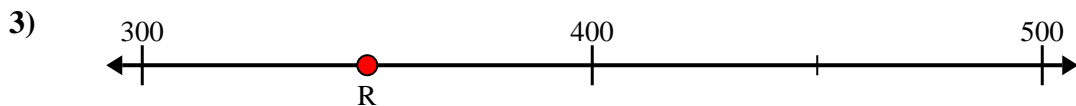


3. _____

4. _____

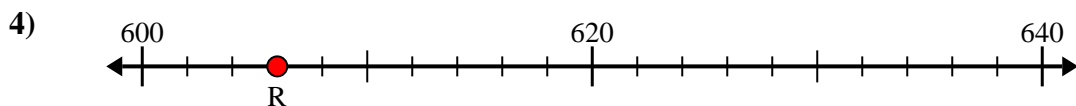


5. _____

6. _____

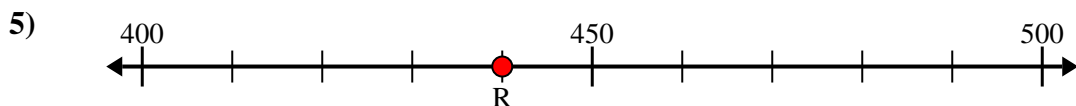





7. _____

8. _____

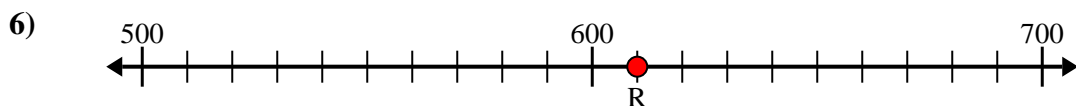











9. _____

10. _____

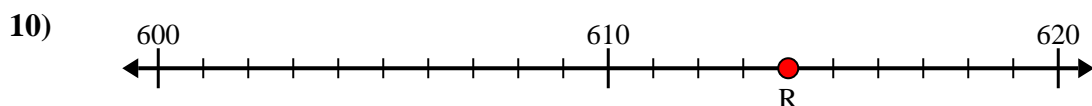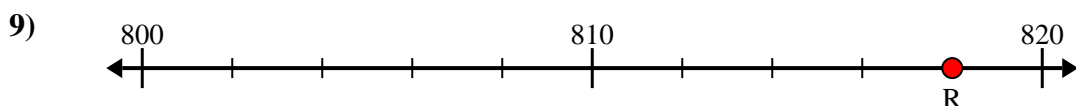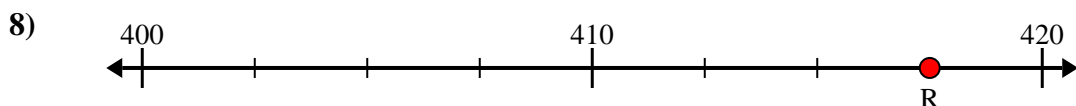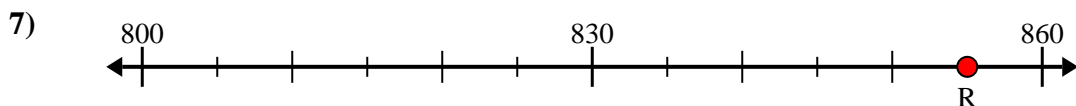



Find the value of R.

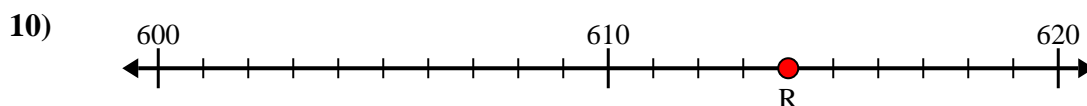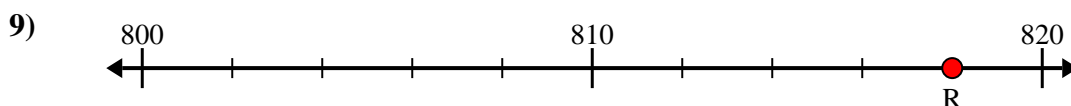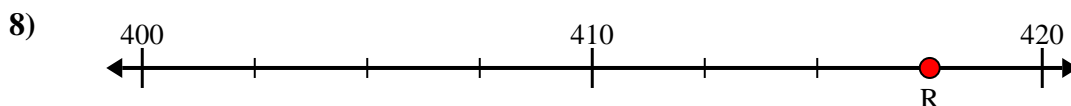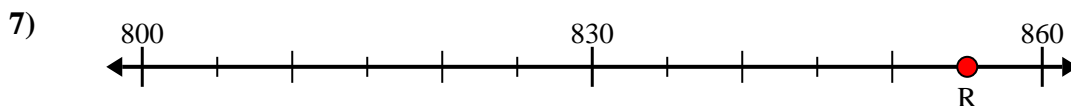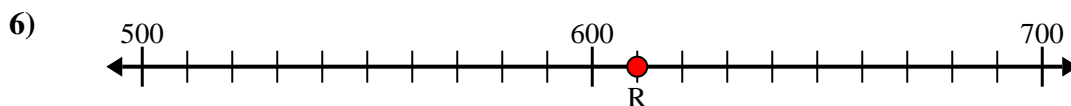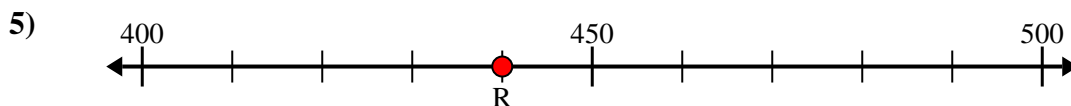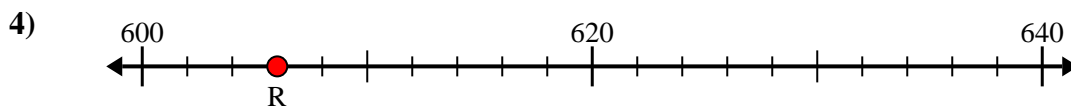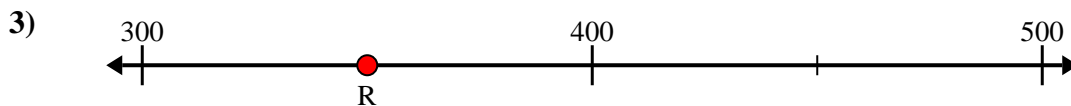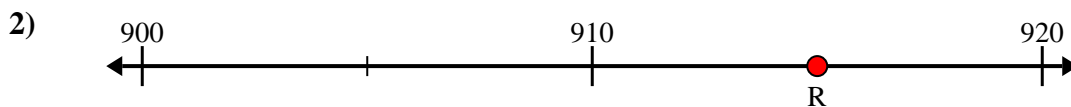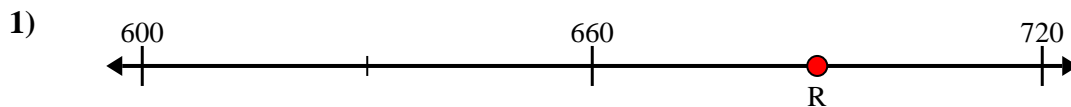**Answers**1. **690**2. **915**3. **350**4. **606**5. **440**6. **610**7. **855**8. **417.5**9. **818**10. **614**